



## VE215 2023Su Assignment 2

Due Date: 23:59, June 3rd, 2023

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.
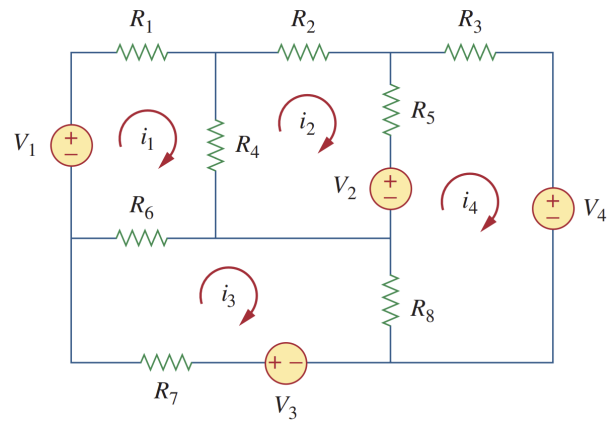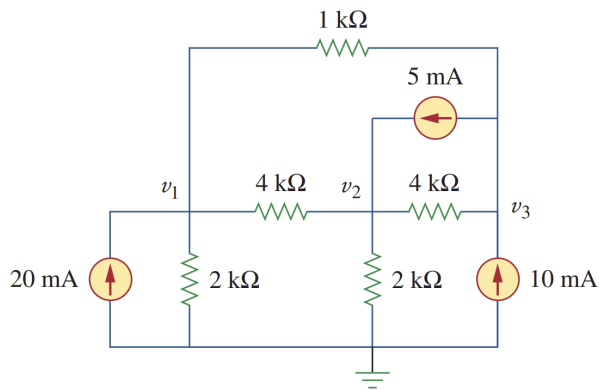
### Exercise 2.1 (30%)


Solve the voltages of the first circuit, and the currents of the second circuit, by inspection.



## VE215 2023Su Assignment 2
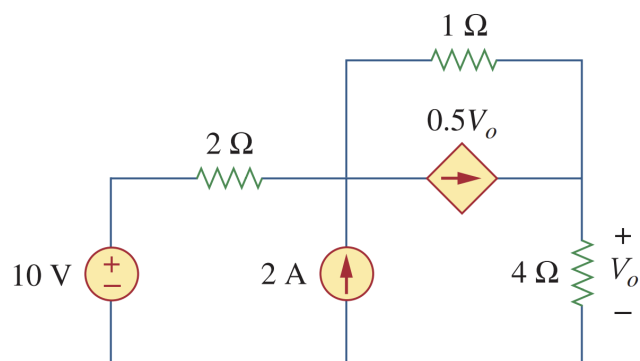
### Exercise 2.2 (15%)


Use superposition to find  $V_o$  in the circuit below.



## VE215 2023Su Assignment 2

### Exercise 2.3 (35%)

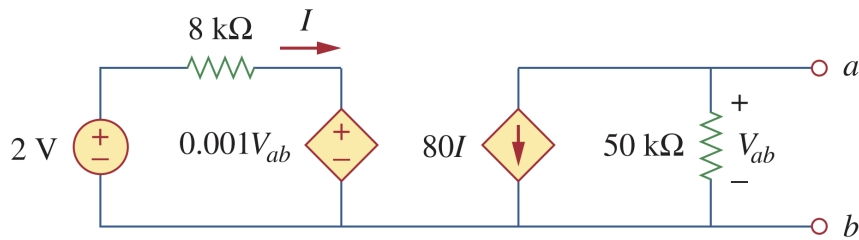- (a) (20%) Obtain the Thevenin and Norton equivalent circuit at the terminal a-b. Draw the circuit.
- (b) (5%) Calculate the voltage  $V_{ab}$  if now a resistor of  $10k\Omega$  connects between terminal a-b.
- (c) (10%) Calculate the maximum power transferred to a resistor that connects between terminal a-b. Also calculate the resistance of that resistor.



## VE215 2023Su Assignment 2

### Exercise 2.4 (20%)

Calculate the maximum power that can be delivered to the variable resistor  $R$  in the following circuit.

