

# VE215 RC5

Erdao Liang, Chongye Yang

UM-SJTU JI

July 13, 2023

# Overview

## AC Power Analysis

Instantaneous Power

Maximum Average Power Transfer

Effective or RMS Value

Complex Power

Power Factor Correction

# Instantaneous and Average Power

Both  $v(t)$  and  $i(t)$  here are instantaneous values. (not rms)

$$p(t) = v(t) \cdot i(t)$$

Sinoidal

Instantaneous power:

$$\begin{aligned} p(t) &= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) \\ &= \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\delta} + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \end{aligned}$$

# Average Power

General definition:

$$P = \frac{1}{T} \int_0^T p(t) dt$$

For sinusoids,

$$P = \frac{1}{2} \underline{V_m I_m \cos(\theta_v - \theta_i)}$$

Represented with phasor  $\tilde{V}$  and  $\tilde{I}$ ,

$$P = \underline{\frac{1}{2} \text{Re}(\tilde{V} \tilde{I}^*)}$$

## Average Power

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

- ▶ when  $\theta_v - \theta_i = 0$ , purely resistive load  $R$ .

always true

$$P = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{V_m^2}{R}$$

(the second equality not true when  $\theta_v - \theta_i \neq 0$ )

- ▶ when  $|\theta_v - \theta_i| = 90^\circ$ , purely reactive load  $X$ . It absorbs no **average** power.
- ▶ Generally,

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*) = \frac{1}{2} \operatorname{Re}((\tilde{I} Z) \tilde{I}^*) \\ &= \frac{1}{2} \operatorname{Re}(I^2 R + j I^2 X) = \frac{1}{2} I_m^2 R \end{aligned}$$

(Only resistance contributes to the average power absorbance)

# Maximum Average Power Transfer

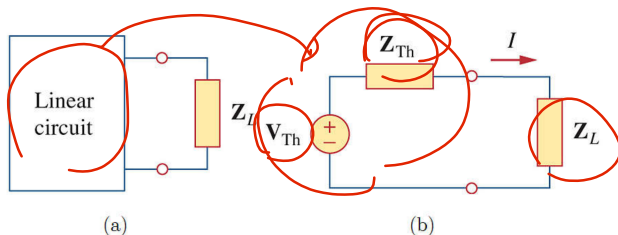


Figure 11.7 Finding the maximum average power transfer  
(a) circuit with a load, (b) the Thevenin equivalent.

- If there is no restriction on  $Z_L$ ,

$$\underline{R_L = R_{Th}} \quad \underline{X_L = -X_{Th}} \quad \left| P_{max} = \frac{|V_{Th}^2|}{8R_{Th}} \right|$$

- If  $Z_L$  is purely resistive,

$$\left| R_L = \sqrt{R_{Th}^2 + X_{Th}^2} \right| \quad P_{max}$$

# Effective or RMS Value

Definition: The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current (similarly for voltage).

$$I_{\text{eff}}^2 R = \frac{R}{T} \int_0^T i^2 dt$$

Effective value = RMS (root mean square) value.

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{\text{eff}}$$
$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2 dt} = V_{\text{eff}}$$

## Effective or RMS Value

$$P = \frac{1}{2} I_m^2 R$$

$$I_{rms}^2 \cdot R$$

- ▶ Avg power absorbed by a circuit element (generally true):

$$P = I_{rms}^2 R = V_{rms}^2 \frac{R}{R^2 + X^2}$$

$$P = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*) = \operatorname{Re}(\tilde{V}_{rms} \tilde{I}_{rms}^*) = \frac{1}{2} I_m^2 R = I_{rms}^2 R = \frac{1}{2} V_m^2 \operatorname{Re}\left(\frac{1}{Z^*}\right) = V_{rms}^2 \frac{R}{R^2 + X^2}$$

- ▶ RMS value for a sinusoid **sinusoid**:

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad V_{rms} = \frac{V_m}{\sqrt{2}}$$

- ▶ Average power absorbed by an element in a **sinusoidal** circuit:

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P = \left(\frac{1}{2}\right) V_m I_m \cos(\quad)$$




## Effective or RMS Value

**Caution: from now on, unless specified, all values will be assumed to be RMS values.**

# Complex Power

We define this “complex power” that includes all the information.

$$\begin{aligned}\text{Complex Power} = \tilde{S} &= \tilde{V}_{rms} \tilde{I}_{rms}^* = |I_{rms}| |V_{rms}| \angle(\theta_v - \theta_i) \\ &= |\tilde{S}| \angle(\theta_v - \theta_i) \text{ (polar form)} \\ &= \underline{P} + j\underline{Q} \text{ (rectangular form)} \quad \underline{\underline{VA}}\end{aligned}$$

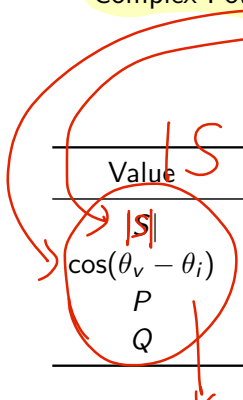

Value	Name	Meaning	Unit
$ \tilde{S} $	Apparent power	Magnitude of $\tilde{S}$	VA
$\cos(\theta_v - \theta_i)$	Power factor	Cosine of angle of $\tilde{S}$	/
$P$	<u>Real power</u>	Real part of $\tilde{S}$	W
$Q$	Complex power	Imaginary part of $\tilde{S}$	VAR

$(\theta_v - \theta_i) = \text{pf angle}$

# Complex Power

- Complex power

$$\tilde{S} = \tilde{V}_{rms} \tilde{I}_{rms}^* = |I_{rms}| |V_{rms}| \angle(\theta_v - \theta_i) = |S| \angle(\theta_v - \theta_i) = P + jQ$$

$$\tilde{S} = |I_{rms}|^2 Z = \frac{|V_{rms}|^2}{Z^*}$$

- Apparent power

$$|S| = |V_{rms}| |I_{rms}| = |I_{rms}|^2 |Z| = \sqrt{P^2 + Q^2}$$

- Real power

$$P = \text{Re}(\tilde{S}) = |S| \cos(\theta_v - \theta_i) = |I_{rms}|^2 R$$

- Complex power

$$Q = \text{Im}(\tilde{S}) = |S| \sin(\theta_v - \theta_i) = |I_{rms}|^2 X$$

- Power factor

$$\text{pf} = \frac{P}{|S|} = \cos(\theta_v - \theta_i)$$

# Complex Power

$$\frac{P}{|S|}$$

Power factor  $\text{pf} = \frac{P}{|S|} = \cos(\theta_v - \theta_i)$ :

- ▶  $\theta_v - \theta_i < 0$ : leading pf
- ▶  $\theta_v - \theta_i > 0$ : lagging pf

Since  $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v)$ , the pf value only tells part of the story. Every time you are asked for a power factor, **you must declare whether it is leading or lagging.**


# Complex Power

We can use the sign of pf angle or  $Q$  to identify the property of the circuit and the loads:



	(1)	(2)	(3)
pf Angle	$\theta_v - \theta_i = 0$	$\theta_v - \theta_i < 0$	$\theta_v - \theta_i > 0$
Sign of $Q$	$Q = 0$	$Q < 0$	$Q > 0$
Properties	Unity pf $I, V$ in phase $X = 0$ Resistive loads	Leading pf $I$ leads $V$ $X < 0$ Capacitive loads	Lagging pf $I$ lags $V$ $X > 0$ Inductive loads

# Complex Power

$$\mathbf{S} = |I_{rms}|^2 \mathbf{Z}$$

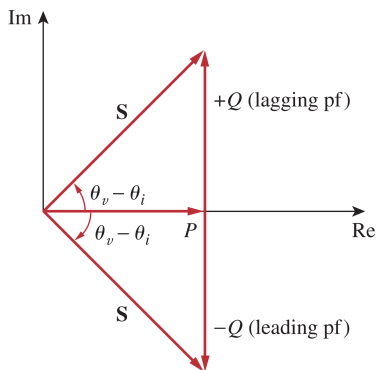

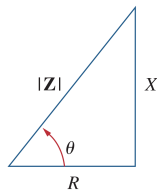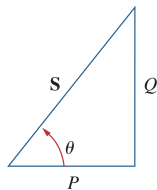And observe that the power factor angle is equal to the angle of the impedance of that part of the circuit.




Exercise 1  $|S| = |\underline{I}_{rms}| \cdot |\underline{V}_{rms}| = \frac{4}{\sqrt{2}} \cdot \frac{120}{\sqrt{2}} = 240$   
 $pf = \cos(\theta_v - \theta_i) = \cos(-20^\circ - 10^\circ) = 0.866$   
Pf is leading.

$Z$

**Question:**

A series-connected load draws a current  $i(t) = 4\cos(100\pi t + 10^\circ)A$  when the applied voltage is  $v(t) = 120\cos(100\pi t - 20^\circ)V$ . Find the apparent power and the power factor of the load. Determine the element values that form the series-connected load.

$|S|$   
 $Z = \frac{\underline{\tilde{V}}}{\underline{\tilde{I}}} = (25.98 + j15)\Omega$   
 $R$   
 $X < 0$   
 $R = 25.98\Omega$   
 $X_C = -\frac{1}{\omega C}$   
 $C =$



The diagram shows a series circuit with a resistor R and a capacitor C connected to an AC voltage source. The current i(t) flows through the circuit.

# Exercise 1

## Solution:

The apparent power is

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = 240 \text{ VA}$$

The power factor is

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(-20^\circ - 10^\circ) = 0.866 \quad (\text{leading})$$

The pf is leading because the current leads the voltage. The pf may also be obtained from the load impedance.

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15 \, \Omega$$
$$\text{pf} = \cos(-30^\circ) = 0.866 \quad (\text{leading})$$

The load impedance  $\mathbf{Z}$  can be modeled by a 25.98- $\Omega$  resistor in series with a capacitor with

$$X_C = -15 = -\frac{1}{\omega C}$$

or

$$C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 212.2 \, \mu\text{F}$$




# Power Factor Correction

$P_f$  ↗


$$\underline{Z = R + jX \downarrow}$$

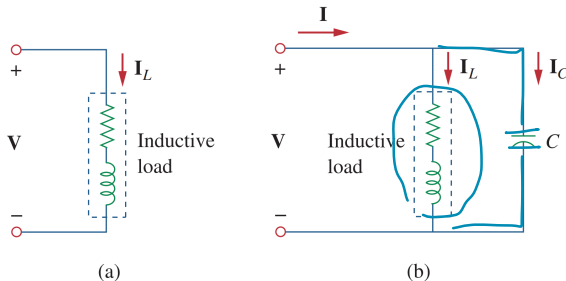- ▶ Goal: increase the pf of a load → make it less inductive → reduce energy loss
- ▶ Solution: add a capacitor in parallel to the load


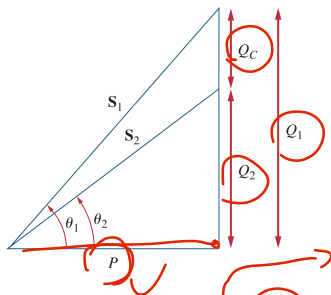
# Power Factor Correction

Goal: increase the pf from  $\cos \theta_1$  to  $\cos \theta_2$ .



Initial:

$$P = |S_1| \cos \theta_1$$

$$Q_1 = |Q_1| \sin \theta_1 = P \tan \theta_1$$

The "after" we expect:

$$P = |S_2| \cos \theta_2$$

$$Q_2 = |Q_2| \sin \theta_2 = P \tan \theta_2$$

Since  $Q_c (= Q_1 - Q_2) = \frac{V_{rms}^2}{X_c}$ , then the value of the required capacitance  $C$  is

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{Q_2 - Q_1}{\omega V_{rms}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

## Exercise 2

**Question:**

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance necessary to raise the pf to 0.95.

## Exercise 2

### Question:

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance necessary to raise the pf to 0.95.

Formula:  $C = \frac{P \tan(\theta_1) - \theta_2}{\omega \cdot V_{rms}^2}$

$$\theta_1 = \cos^{-1}(0.8)$$

Answer: 310.5  $\mu$ F

# References

1. 2023 Summer VE215 slides, Rui Yang
2. Fundamentals of Electric Circuits, 5th e, Sadiku, Matthew
3. 2022 Fall RC5, Yuxuan Peng
4. 2022 Fall RC6, Zhiyu Zhou

Thank you!