

# VE215 2023Su Assignment 8


Due Date: 23:59, August 3rd, 2023

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

## Exercise 8.1 (30%)

For the circuit shown below, find the transfer function

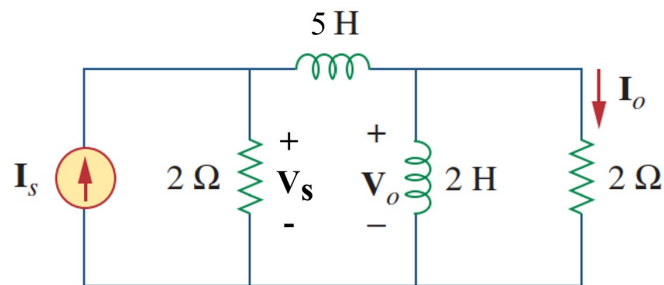
- (a) (15%)  $I_o(\omega)/I_s(\omega)$ , and its zeros and poles.
- (b) (15%)  $V_s(\omega)/I_s(\omega)$ , and its zeros and poles.




## VE215 2023Su Assignment 8
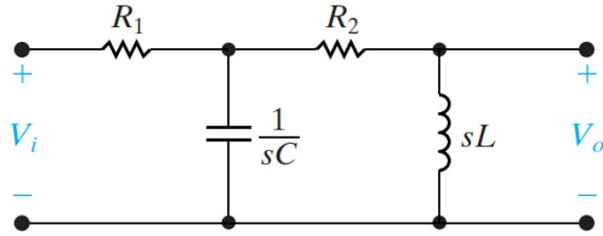
### Exercise 8.2 (30%)

Find  $H(s) = V_o(s)/V_i(s)$ , where  $s = j\omega$  in both circuits. Assume that  $R_1 = R_2 = R_3 = 100\Omega$ ,  $L = 1\text{H}$  and  $C = 1\text{mF}$  for (a) and (b).



(a)

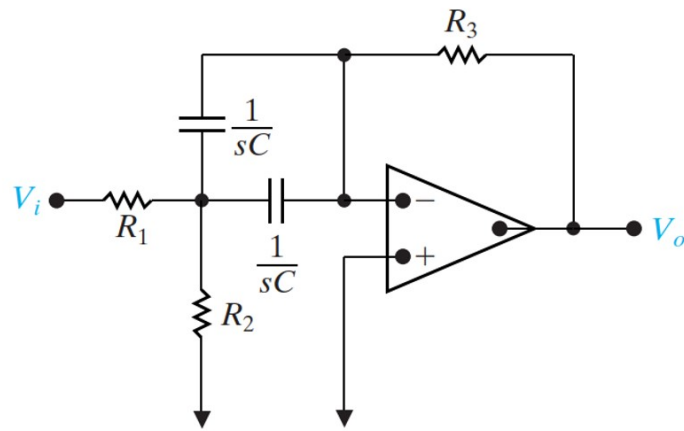

(b)

# VE215 2023Su Assignment 8

## Exercise 8.3 (40%)

Obtain the Bode plots ( $H - \omega$  and  $\phi - \omega$  relationship) for

(a) (20%)

$$H(j\omega) = \frac{0.1(20 + j\omega)}{j\omega(5 + j\omega)}$$

(b) (20%)

$$H(j\omega) = \frac{100(1 + j\omega)}{j\omega(-\omega^2 + 10j\omega + 25)}$$