




# VE215 2023Su Assignment 5

Due Date: 23:59, July.4th, 2023

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

## Exercise 3.1 (30%)

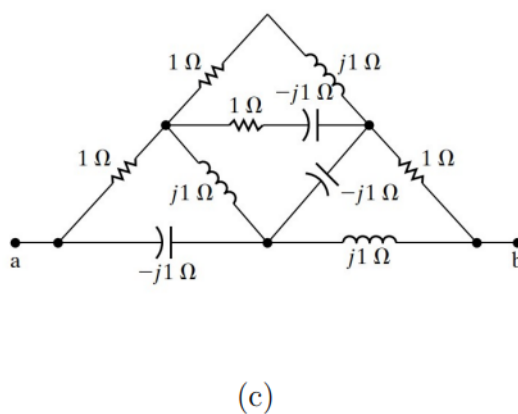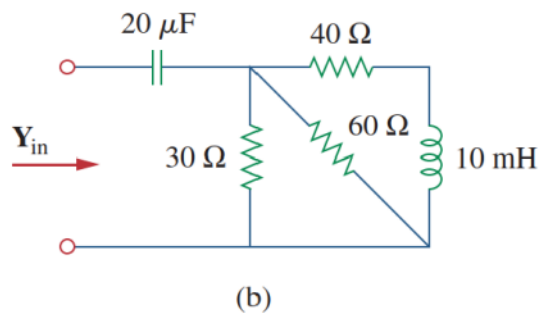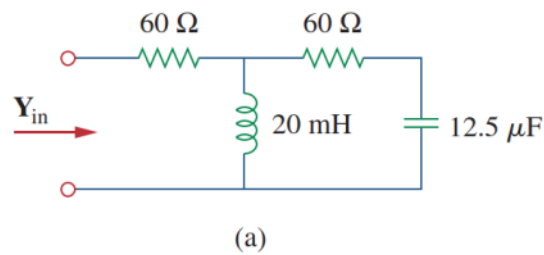
- (a) (10%) Find the equivalent admittance of the circuits at  $\omega = 50 \text{ rad/s}$ .
- (b) (10%) Find the equivalent admittance of the circuits at  $\omega = 50 \text{ rad/s}$ .
- (c) (10%) Find the equivalent impedance  $Z_{ab}$ .




## VE215 2023Su Assignment 5

### Exercise 3.2 (30%)

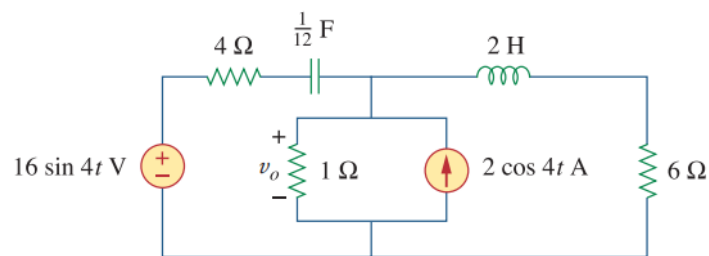(a) (15%) Determine  $v_o$  in the circuit below.



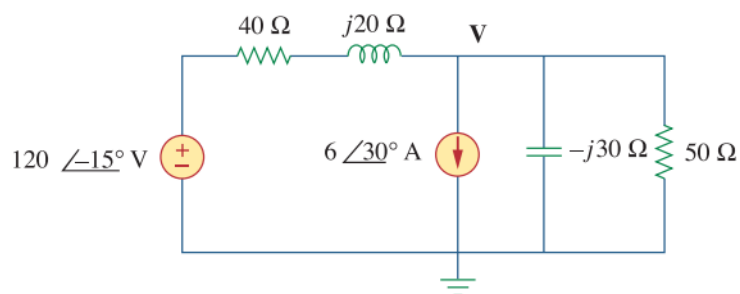
(b) (15%) Use nodal analysis to find  $\mathbf{V}$  in the circuit below.



## VE215 2023Su Assignment 5

### Exercise 3.3 (40%)

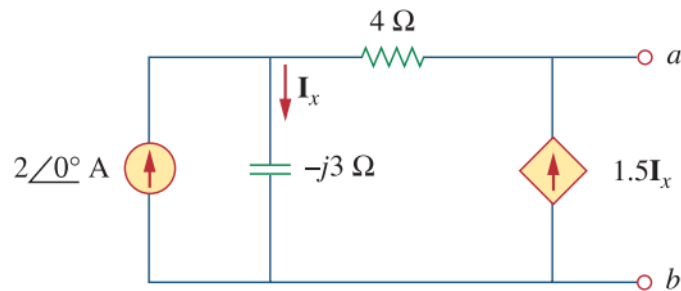(a) (20%) Find the Thevenin equivalent at terminal a-b of the circuit below. And also draw the phasor diagram of the Thevenin equivalent impedance.



(b) (20%) Find the Norton equivalent at terminal a-b of the circuit below. And also draw the phasor diagram of the Norton equivalent impedance. Take  $\omega = 10 \text{ rad/s}$ .

